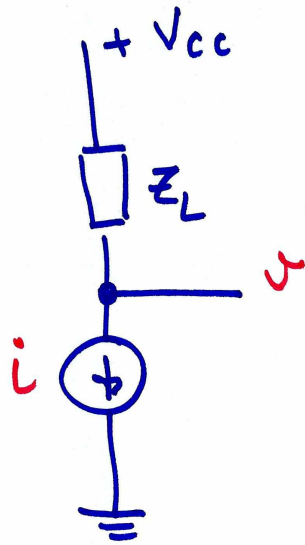



## Amplificadores de banda estrecha



$Z_L \equiv$  Impedancia de carga

$i \equiv$  corriente del dispositivo activo

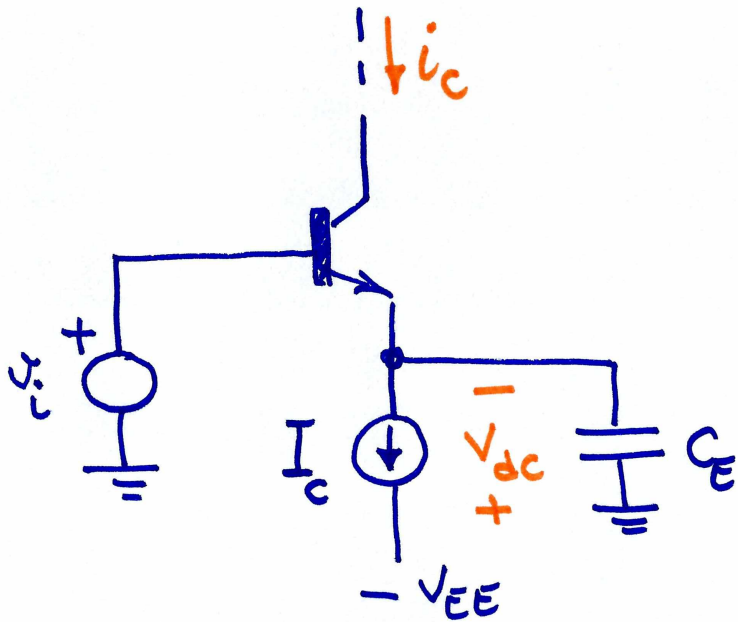$i$  es función de la señal que queremos amplificar.



$$v_i = V_1 \cos \omega_0 t$$

$$\begin{cases} v_{BE} = V_{dc} + V_1 \cos \omega_0 t \\ i_c = I_s e^{v_{BE}/V_T} \end{cases}$$

$$i_c = I_C + I_C \sum_k a_k \cos k \omega_0 t$$


$$= I_C + G_m V_1 \cos \omega_0 t + \text{armònics}$$

$$\text{Si } x \equiv \frac{v_i}{V_T} \quad \text{donde } V_T = \frac{kT}{q} \approx 25\text{mV}$$

$$G_m = G_m(x) \equiv \text{transconductancia}$$

$$\underline{\text{Si } x \rightarrow 0} \quad G_m(x) \rightarrow g_m = \frac{I_c}{V_T}$$




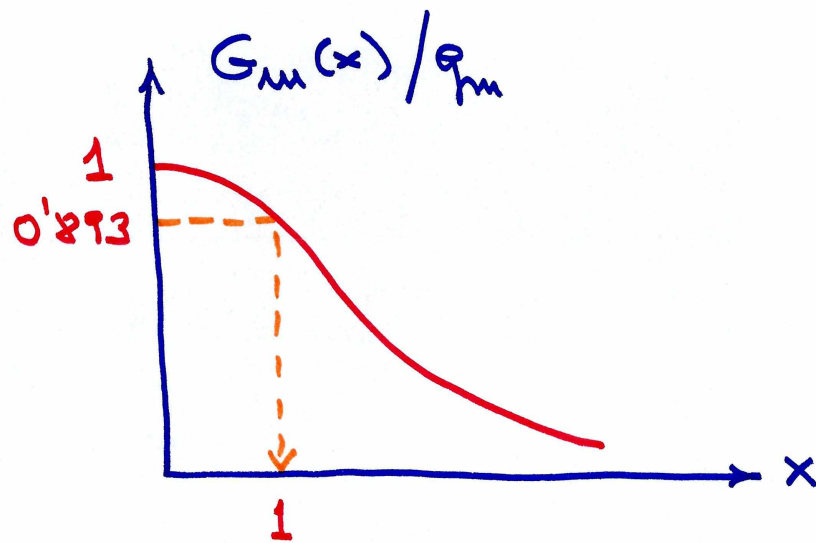
$$\Rightarrow \left\{ \begin{array}{l} i_c = I_c + g_m v_i \\ \Delta i_c = g_m v_i \end{array} \right.$$



Si  $x < 1$   
 $G_m \approx g_m$

### Conclusiones

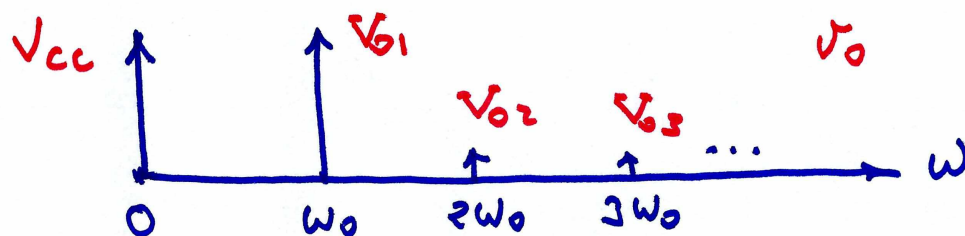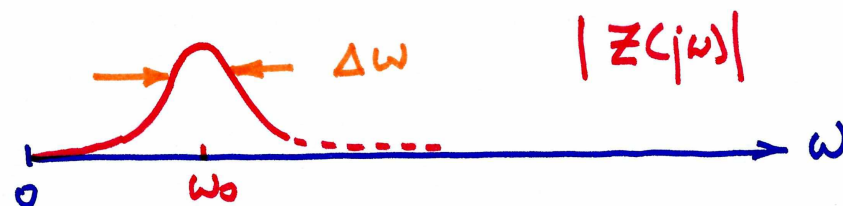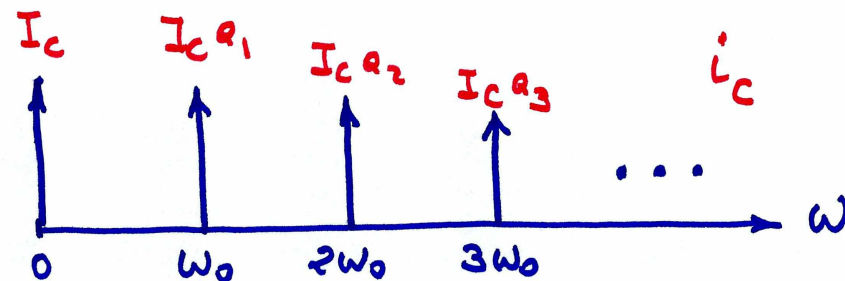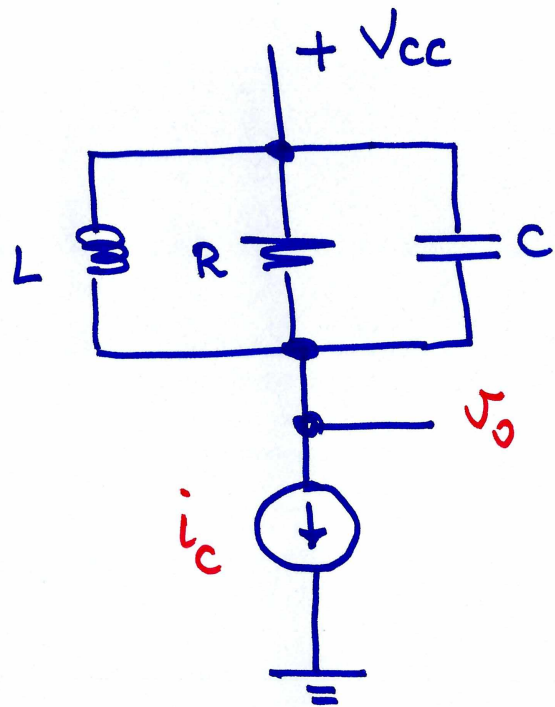- (1) Si  $x \leq 0.1 \rightarrow \Delta i_c$  es proporcional a  $v_i$
- (2) Si  $x < 1 \rightarrow i_c$  tiene un armónico proporcional a  $v_i$ , pero hay otros armónicos



$$V_{o1} = I_c a_1 |Z|_{\max} = G_m |Z|_{\max} V_i$$

Si  $\Delta\omega \ll \omega_0 \Rightarrow v_o(t) \approx V_{cc} - G_m |Z|_{\max} v_i$

# Distorsión

$$\begin{aligned} \underline{2^\circ \text{ armónico}} &= \frac{V_{o2}}{V_{o1}} \cdot 100\% \\ &= \frac{Q_2 |Z(2j\omega_0)|}{Q_1 |Z(j\omega_0)|} \cdot 100\% \end{aligned}$$

