


Producto GxBW

SIN REALIMENTAR

$G_{x}BW = cte = 1MHz (741)$


Ej: 741

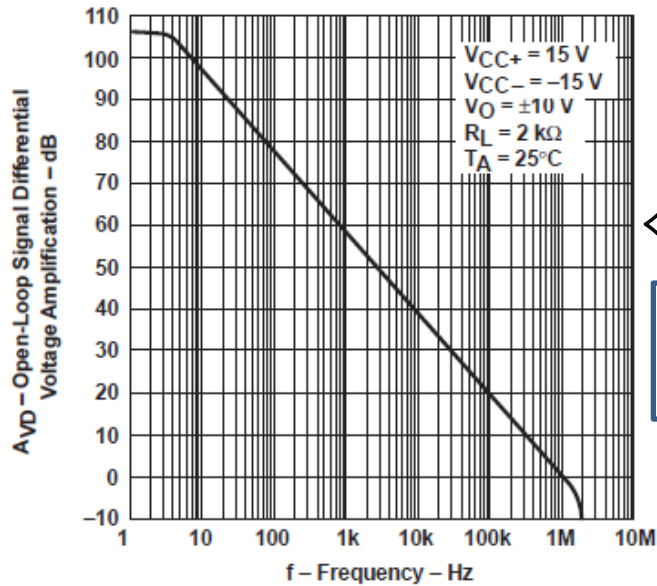OPEN-LOOP LARGE-SIGNAL DIFFERENTIAL VOLTAGE AMPLIFICATION vs FREQUENCY



Sistema de primer orden (1 solo polo)
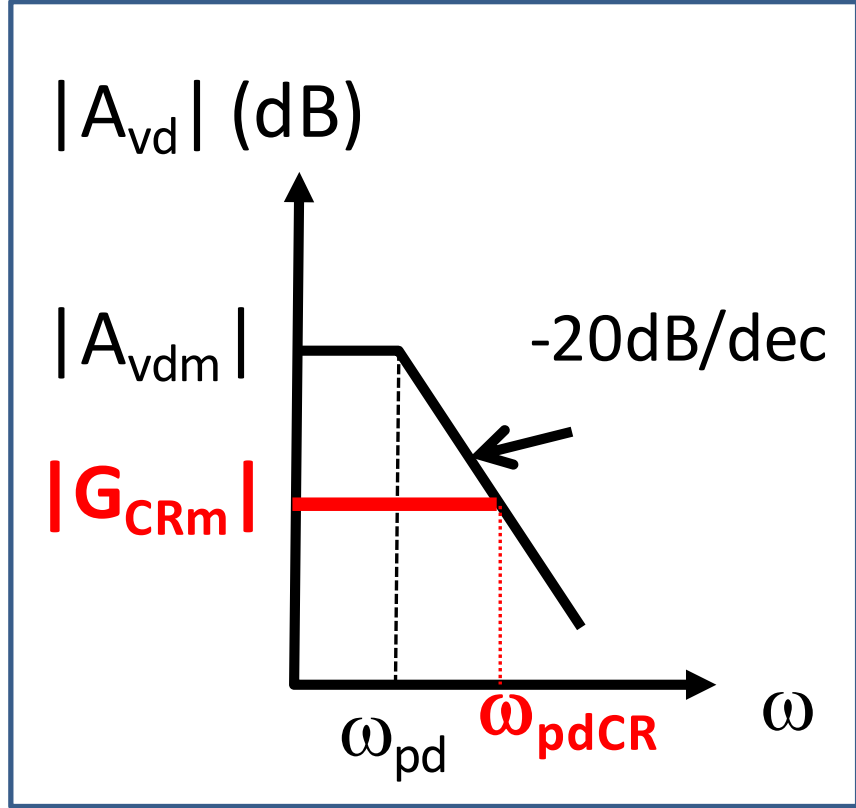
$$A(j\omega) = \frac{A_{vdm}}{1 + j\omega/\omega_{pd}}$$




CON REALIMENTACIÓN NEGATIVA



$$G_{CR}(j\omega) = \frac{A}{1 + A\beta} = \frac{\frac{A_{vdm}}{1 + j\omega/\omega_{pd}}}{1 + \left(\frac{A_{vdm}}{1 + j\omega/\omega_{pd}}\right) \cdot \beta} = \frac{\frac{A_{vdm}}{1 + A_{vdm} \cdot \beta}}{1 + j\omega/\omega_{pd} \cdot (1 + A_{vdm} \cdot \beta)}$$

G_{CRm} (pointing to the numerator) and ω_{pdCR} (pointing to the denominator)

Modo monoestable


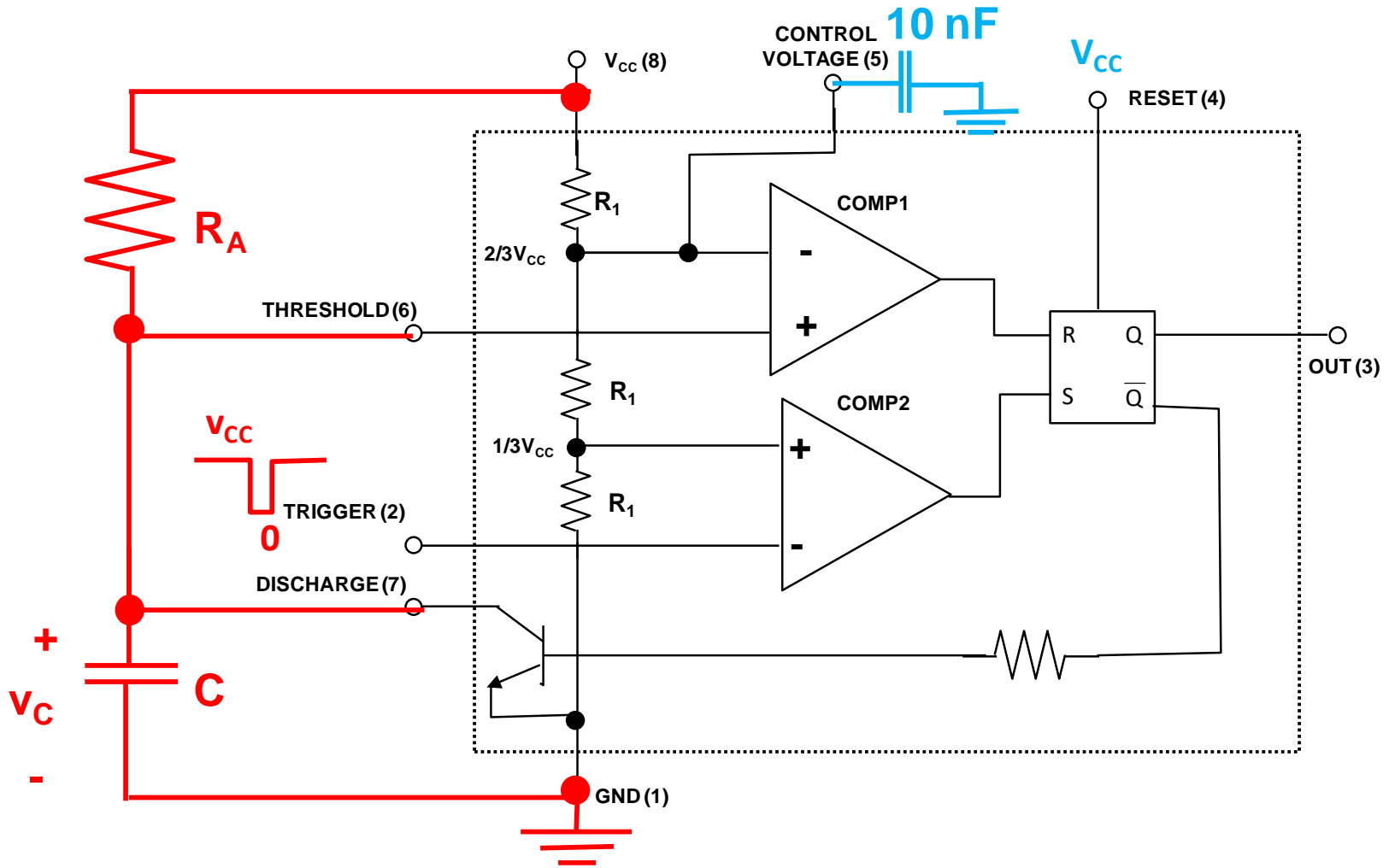


Modo monoestable

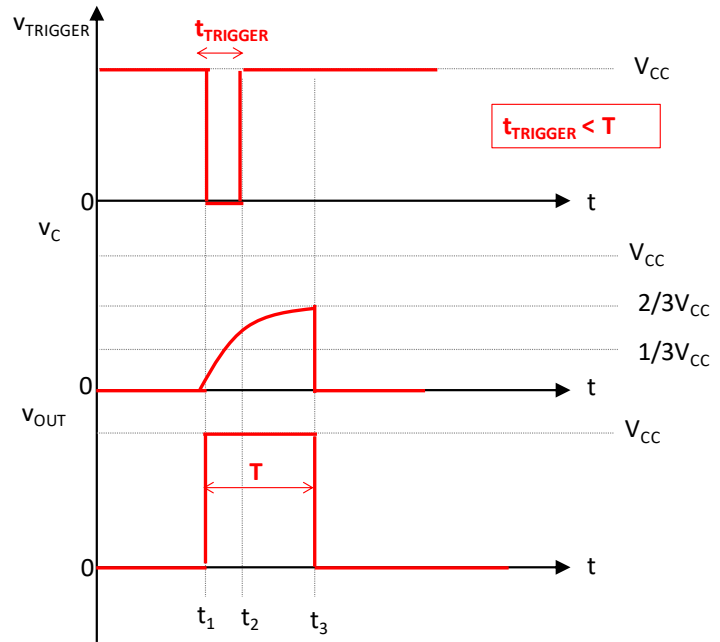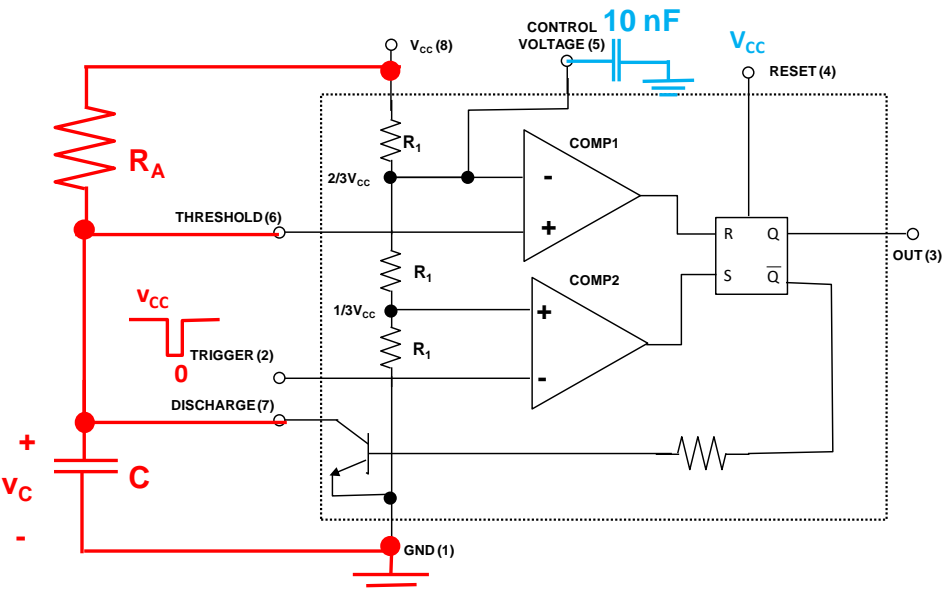

$v_C(0) = 0; V_{out}(0) = 0$


	COMP1			COMP2					
t	V ₊	V ₋	R	V ₊	V ₋	S	V _{OUT}	\overline{Q}	v _C
[0-t ₁)	0	2/3V _{CC}	0	1/3V _{CC}	V _{CC}	0	0	1	0
t ₁	0	2/3V _{CC}	0	1/3V _{CC}	0	1	1	0	v _C (t)
(t ₁ -t ₂)	v _C (t)	2/3V _{CC}	0	1/3V _{CC}	0	1	1	0	v _C (t)
[t ₂ -t ₃)	v _C (t)	2/3V _{CC}	0	1/3V _{CC}	V _{CC}	0	1	0	v _C (t)
t ₃	↑2/3V _{CC}	2/3V _{CC}	1	1/3V _{CC}	V _{CC}	0	0	1	0
>t ₃	0	2/3V _{CC}	0	1/3V _{CC}	V _{CC}	0	0	1	0

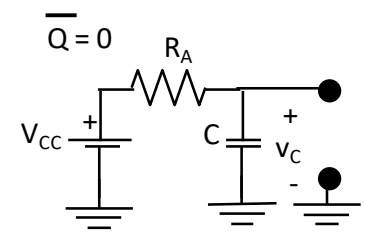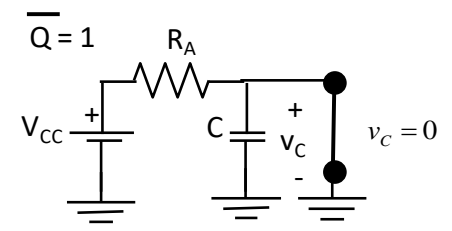


$$v_C(t) = v_{C(t \rightarrow \infty)} + (v_{C(t=0)} - v_{C(t \rightarrow \infty)}) e^{-\frac{t}{\tau}} \quad 5$$

REAL

Integrador

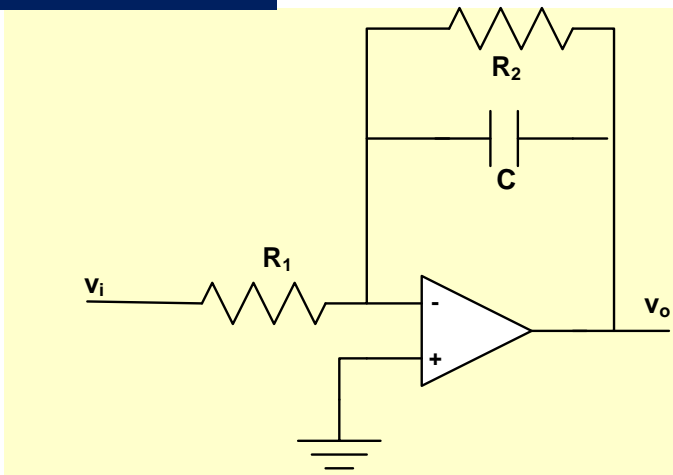

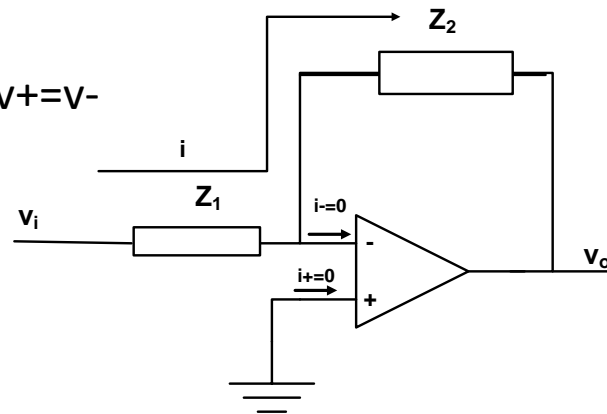- Cortocircuito virtual: $v_+ = v_-$
- $i(Z_1) = i(Z_2) = i$




$$\frac{V_o}{V_i}(j\omega) = -\frac{Z_2}{Z_1} = -\frac{1 + j\omega R_2 C}{R_1} = \frac{\frac{R_2}{R_1}}{1 + j\omega R_2 C}$$


Polo: $\omega_c = \frac{1}{R_2 C}$

$|v_o/v_i(j\omega)|$ (dB)

$20\log(R_2/R_1)$

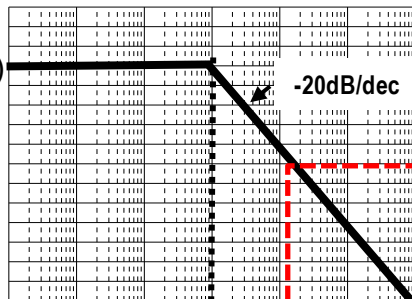


$\angle v_o/v_i(j\omega)$ (°)

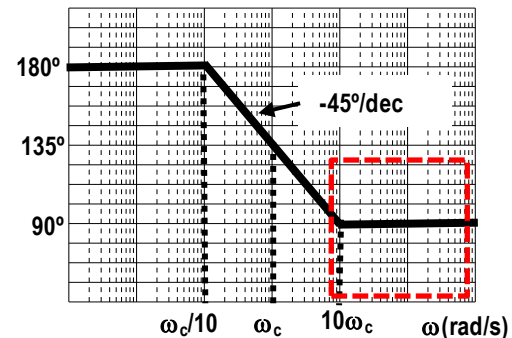

Integra si $\omega \gg 1/R_2 C$

$$\frac{v_o}{v_i} \Big|_{BF} \rightarrow -\frac{R_1}{R_2}$$

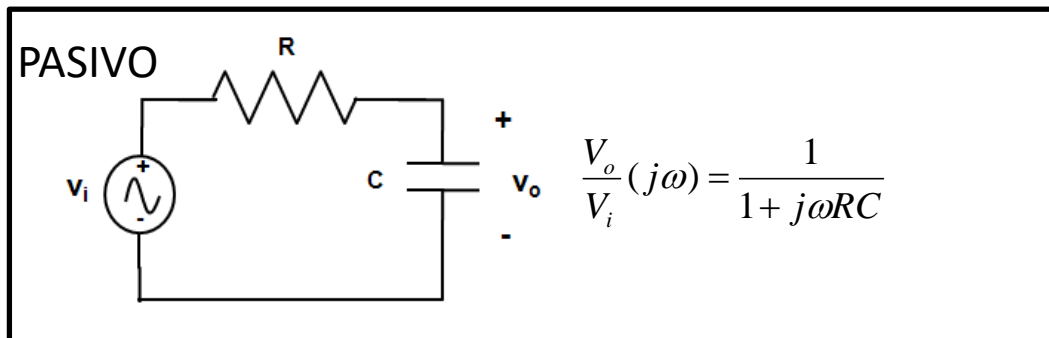

Datos PLL:

F(s) = 1; Ganancia de lazo del PLL: $K_V = K_d \cdot A_V \cdot K_O = 500 \text{ s}^{-1}$; Margen de enganche PLL: $\Delta f_L = \pm 125 \text{ Hz}$
 Ganancia del VCO: $K_O = 2\pi \cdot \text{krad/s.V}$; Frecuencia de oscilación libre del VCO: $\omega_{fr} = 2\pi \cdot 500 \text{ rad/s}$


$$v_i(t) = \text{sen}(\omega_i \cdot t) = \text{sen}\{\omega_p \cdot [1 + m \cdot x_m(t)] \cdot t\} = \text{sen}\{2\pi \cdot 500 \cdot [1 + 0.1 \cdot \text{sen}(2\pi \cdot 5 \cdot t)] \cdot t\} : \text{Señal FM}$$

$$\Rightarrow \omega_i(t) = 2\pi \cdot 500 + 2\pi \cdot 50 \cdot \text{sen}(2\pi \cdot 5 \cdot t) \rightarrow \begin{cases} f_{i\text{máx}} = 550 \text{ Hz} \\ f_{i\text{mín}} = 450 \text{ Hz} \end{cases}$$


Respuesta en frecuencia ($\Delta\omega_i$ sinusoidal)

$$\frac{v_e}{\Delta\omega_i}(s) = \frac{K_V / K_O}{s + K_V}$$

$|v_e/\Delta\omega_i(j\omega)|$

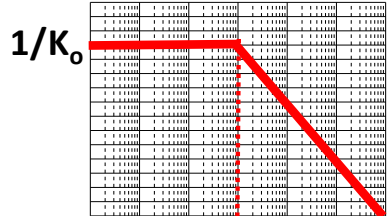

$\angle v_e/\Delta\omega_i(j\omega)$

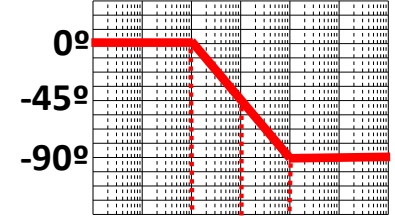



K_V $\omega(\text{rad/s})$ $K_V/10$ K_V $10K_V$ $\omega(\text{rad/s})$

- Margen de enganche PLL: $\Delta f_L = \pm 125 \text{ Hz}$

$$f_{iL\text{máx}} = f_{fr} + \Delta f_L = 500 \text{ Hz} + 125 \text{ Hz} = 625 \text{ Hz} > f_{i\text{máx}}$$

$$f_{iL\text{mín}} = f_{fr} - \Delta f_L = 500 \text{ Hz} - 125 \text{ Hz} = 375 \text{ Hz} < f_{i\text{mín}}$$

Rectificadores de precisión

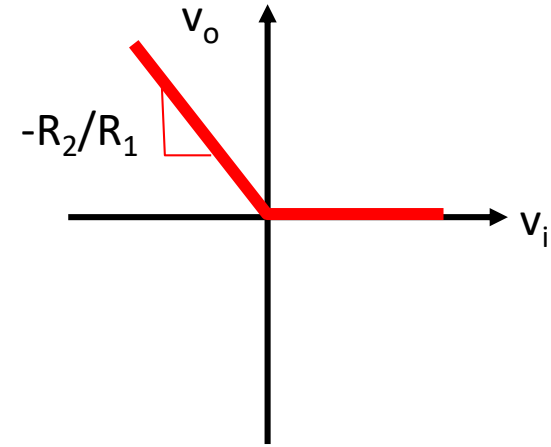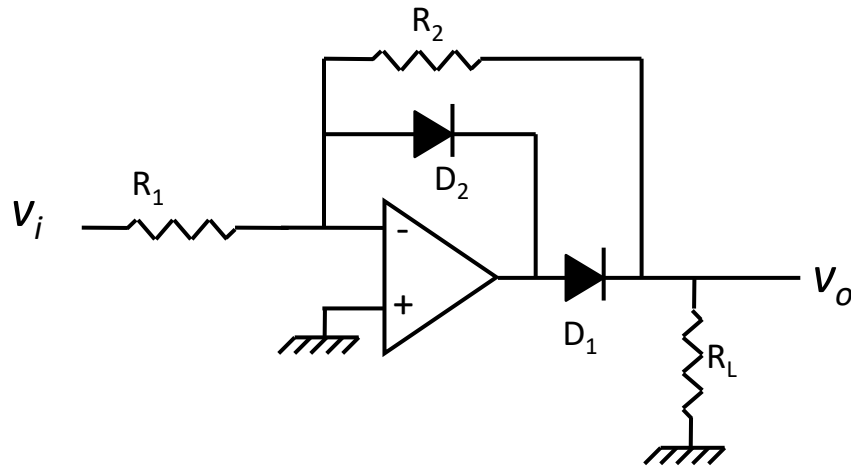

$$v_i > 0 \Rightarrow \begin{cases} D_2 & \text{ON} \\ D_1 & \text{OFF} \end{cases}$$

$$v_i < 0 \Rightarrow \begin{cases} D_2 & \text{OFF} \\ D_1 & \text{ON} \end{cases}$$

